

```

% % % % % Part 4
% %
% % A) If the output voltage was changed to a non-linear representation for
% the current it would have to be represented in the B matrix of the MNA
% form
%
% B) the B matrix would have to be included when making the calculation.
% instead of using the the  $a/R3$  and denoting there is a voltage at that
% point in the matrix (denoted by the 1 in the fourth column in the last
% row in the G matrix). Just a 1 is denoted so as to allow the B matrix use
% it. Now since we know that the total current is equal to  $a*V3/R3$  we use
% that in the B matrix. Then we use a jacobian to find the non-linear
% solution. begin by defining an operating point.
%

%C)
clear all
close all

R1 = 1;
C = 0.25;
R2 = 2;
L = 0.2;
R3 = 10;
a = 100;
R4 = 0.1;
Ro = 1000;
Y1 = 1/R1;
Y2 = 1/R2;
Y3 = 1/R3;
Y4 = 1/R4;

% V = [V1    V2          V3    V4    V5          i1  iL  i3];
G = [-1/R1  1/R1          0      0      0          1   0   0;
      1/R1  (-1/R1)-(1/R2)  0      0      0          0  -1   0;
      0      0          -1/R3   0      0          0   1   0;
      0      0          0    -1/R4   1/R4          0   0   1;
      0      0          0     1/R4  (-1/R4)-(1/Ro)  0   0   0;
      1      0          0      0      0          0   0   0;
      0      1          -1     0      0          0   0   0;
      0      0          0      1      0          0   0   0]

% V =  [V1  V2  V3  V4  V5  i1  iL  i3];
Cm =  [-C   C   0   0   0   0   0   0;
        C  -C   0   0   0   0   0   0;
        0   0   0   0   0   0   0   0;
        0   0   0   0   0   0   0   0;
        0   0   0   0   0   0   0   0;
        0   0   0   0   0   0   0   0;
        0   0   0   0   0   0  -L   0;
        0   0   0   0   0   0   0   0]

%B = [0 0 0 0 a*(V3/R3) 0 0 0]

```

```

n = 0;
vin = -10:1:10;
V3 = zeros(size(vin));

for Vin = -10:10
    n = n + 1;
    F = [0 0 0 0 0 Vin 0 0];
    B = [0 0 0 0 a*(V3(n)/R3) 0 0 0];
    V = ((G+Cm)\F')+B;

    V3(n) = V(3);
    Vo(n) = V(5);
end

figure(14)
plot(vin,V3)
title('V3')
figure(15)
plot(vin,Vo)
title('Vo')

```

G =

Columns 1 through 7

-1.0000	1.0000	0	0	0	1.0000	0
1.0000	-1.5000	0	0	0	0	-1.0000
0	0	-0.1000	0	0	0	1.0000
0	0	0	-10.0000	10.0000	0	0
0	0	0	10.0000	-10.0010	0	0
1.0000	0	0	0	0	0	0
0	1.0000	-1.0000	0	0	0	0
0	0	0	1.0000	0	0	0

Column 8

0
0
0
1.0000
0
0
0
0

Cm =

Columns 1 through 7

-0.2500	0.2500	0	0	0	0	0
0.2500	-0.2500	0	0	0	0	0
0	0	0	0	0	0	0

0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	-0.2000
0	0	0	0	0	0	0

Column 8

0  
0  
0  
0  
0  
0  
0  
0  
0



